

ASNG

Sunday, February 18, 2024 10:06 AM

1) $B = 0.2 \text{ T}$, $R = 0.16 \Omega$, $l = 1.6 \text{ m}$, $V_t = 94 \text{ V}$



a) $I_{\text{start}} = \frac{V_t}{R} = 335.7143 \text{ A}$

$F_{\text{start}} = B I_{\text{start}} l = 107.4286 \text{ N}$

b) $v_{\text{load}} = \frac{V_t}{B l} = 293.75 \text{ m/s}$

c) $F_{\text{load}} = 25 \text{ N}$ (Given)

$$v_{\text{new}} = \frac{V_t}{B l} - \frac{F_{\text{load}} \cdot R}{(B l)^2} = 275.3906 \text{ m/s}$$

$F_{\text{new}} = F_{\text{start}} - F_{\text{load}} = 82.4286 \text{ N}$

$P_{\text{out}} = V_{\text{bar}} \cdot I_{\text{bar}} = 18578.6192 \text{ W}$

$P_{\text{in}} = V_t \cdot I_{\text{new}} = 24713.3929 \text{ W}$


$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100\% = 76.718\%$

$$I_{\text{bar}} = \frac{F_{\text{new}}}{B l} = 257.5893 \text{ A}$$

$F_{\text{bar}} = B I_{\text{bar}} l = 82.4286 \text{ N}$

$V_{\text{bar}} = I_{\text{bar}} \cdot R = 72.125 \text{ V}$

2)

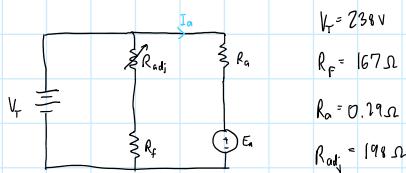

$V_t = 238 \text{ V}$

$P = 41 \text{ hp}$

$E_a = f(I_f)$

$R_a = 0.29 \Omega$

$R_{\text{adj}} = 198 \Omega$

a) $I_{a,\text{start}} = \frac{V_t}{R_a} = 820.6897 \text{ A}$

b) $E_a \uparrow$ $\omega = 1200 \text{ rad/min} (2\pi) = 20(2\pi) \frac{\text{rad}}{\text{s}}$

$k\phi = \frac{E_a}{\omega}$

$I_f = \frac{V_t}{R_{\text{adj}} + R_f} = 0.6521 \text{ A}$

$I_a = \frac{238}{0.29} = \dots$

$T_{\text{start}} \rightarrow k\phi I_a$

$I_f = \frac{238}{167+198} \rightarrow f_a = \dots$

$k\phi w = E_a$

$k\phi = \frac{E_a}{w \cdot 2\pi}$

$T = k\phi I_f$


Linear Interpolation: $E_a = 240.5536 \text{ V}$

$\tau = \frac{E_a}{\omega} I_a$

$= 1591.02 \text{ Nm}$

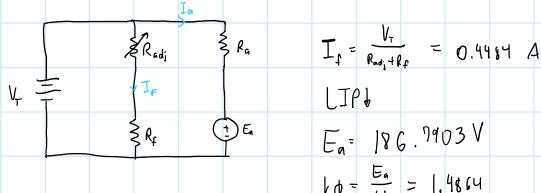3) Shunt DC motor

239 V, $R_f = 199 \Omega$, $R_a = 0.17 \Omega$, $R_{\text{adj}} = 354 \Omega$, $P_{\text{loss}} @ \text{full load} = 2000 \text{ W}$, $\omega = \frac{1200}{60} 2\pi \text{ rad/s} = 40\pi$



$I_a = \frac{V_t}{R_{\text{adj}} + R_f} = 0.4484 \text{ A}$

LIP ↓

$E_a = 186.7903 \text{ V}$

$k\phi = \frac{E_a}{\omega} = 1.4864$

239 V

$P_{\text{out}} + P_{\text{loss}} = 2000 \text{ W}$

$I_f = \frac{239}{179+354} = \dots$

$E_a = \dots$

$k\phi = \frac{E_a}{20\pi} = \dots$

$P_{\text{loss}} = E_a I_f = \dots$

$I_a = \frac{239}{199} = \dots$

$V_a = E_a = \dots$

$I_{\text{idle}} \rightarrow P = P_{\text{loss}}$

System $P_{\text{loss}} = E_{a,\text{idle}} \cdot I_a$

$I_a = \frac{V_t - E_{a,\text{idle}}}{R_a} = 0.4186 \text{ A}$

$E_{a,\text{idle}} = 237.5688 \text{ V} = k\phi w_{\text{idle}}$

$w_{\text{idle}} = 157.9251 \text{ rad/s} \xrightarrow{k\phi} 1526.2075 \text{ rpm}$

$I_a = \frac{V_t - E_a}{R_a} = 309.1160 \text{ A}$

$= k\phi w_{\text{idle}} \cdot I_a$

$w_{\text{idle}} = 4.3811 \text{ rad/s} \xrightarrow{k\phi} 41.8364 \text{ rpm}$

$I_{a,\text{idle}} = \frac{V_t - E_a}{R_a} = \frac{V_t - k\phi w_{\text{idle}}}{R_a} = 1367.5753 \text{ A}$

$$\omega_{idle} = 157.9851 \text{ rad/s} \xrightarrow{\times \frac{2\pi}{2\pi}} 1562.205 \text{ rpm}$$


$$I_T = I_f + I_a = 8.8670 \text{ A}$$

~~$$I_{a_{idle}} = \frac{V_t - E_a}{R_a} = \frac{V_t - k\phi \omega_{idle}}{R_a} = 1367.5953 \text{ A}$$~~

$$I_a = \frac{22^{\circ}}{199} \dots$$



4)

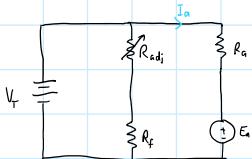

$$233 \text{ V}, R_f = 124, R_a = 0.17, R_{adj} = 200, P = 29 \text{ hp}$$

$$P_{loss} @ full load = 1100 \text{ W}, W = \frac{1200}{60} \cdot 2\pi$$

$$I_f \cdot \frac{V_t}{R_f + R_{adj}} = 0.7191$$

↓ ITP

$$E_a = 252.5631 \text{ V}$$

$$k\phi = \frac{E_a}{W} = 2.0098$$

$$\rho_{tot} = \rho_{loss} = E_{a_{idle}} I_{a_{idle}}$$

$$I_{a_{idle}} = \frac{V_t - E_{a_{idle}}}{R_a} = 4.7374 \text{ V}$$

$$E_{a_{idle}} = 232.1946 \text{ V}$$

$$W_{idle} = \frac{E_{a_{idle}}}{k\phi} = 115.5793 \text{ rad/s}$$

$$\rho_{tot} = \rho_{loss} + \rho_{rated} = E_a I_a$$

$$E_a = k\phi W_{FL} = 215.0265 \text{ V}$$

$$I_a = \frac{V_t - E_{a_{idle}}}{R_a} = 105.9265 \text{ A}$$

$$W_{FL} = 106.9872 \text{ rad/s} \xrightarrow{\times \frac{2\pi}{2\pi}} 1071.6528 \text{ rpm}$$


$$I_s = I_f + I_a = 106.4156 \text{ A}$$

Regulation:

$$\frac{W_{idle} - W_{FL}}{W_{FL}} \times 100\% = 7.98\%$$

$$T = \frac{P_{motor}}{W_{FL}} \cdot \frac{P_{rated}}{W_{FL}} = 202.2110 \text{ Nm}$$

5)

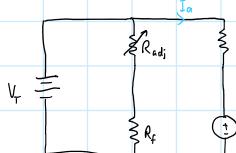

$$V_t = 283 \text{ V}, R_f = 131 \Omega, R_a = 0.11 \Omega, R_{adj} = 157 \Omega, P_{rated} = 21 \text{ hp} = 15666 \text{ W}$$

$$P_{loss} @ FL = 750 \text{ W}, W = 40\pi \text{ rad/s}$$

$$I_f = \frac{V_t}{R_{adj} + R_f} = 1 \text{ A}$$

$$E_a = 280.5412 \text{ V} \rightarrow k\phi = \frac{E_a}{W} = 2.2315$$

$$\rho_{tot} = \rho_{loss} + \rho_{rated} = E_{a_{FL}} I_{a_{FL}}$$

$$I_{a_{FL}} = \frac{V_t - E_{a_{FL}}}{R_a} = 59.3725 \text{ V}$$

$$E_{a_{FL}} = 276.4685 \text{ V}$$

$$W_{FL} = \frac{E_{a_{FL}}}{k\phi} = 123.8394 \text{ rad/s} \xrightarrow{\times \frac{2\pi}{2\pi}} 1182.5791 \text{ rpm}$$

Relation:

Adjustable R_{adj} : $b/w 80 \Omega, 480 \Omega: \downarrow R_{adj}, \downarrow I_f, \downarrow E_a, \uparrow W$

$$\text{MIN: } I_f = \frac{V_t}{80 + R_f} = 1.3412 \text{ A}$$

(labelled MAX in HP Principle) $E_a = 290.9653$

$$k\phi_{min} = \frac{E_a}{W} = 2.3154$$

:

$$E_{a_{FL}} = 276.4685 \text{ V}$$

$$I_{a_{FL}} = 59.3725 \text{ V}$$

$$W_{FL} = 119.4027 \text{ rad/s} \xrightarrow{\times \frac{60}{2\pi}} 1140.2121 \text{ rpm}$$


$$V_{FL} = 117.11510 \text{ V}$$

MAX $I_f = \frac{V_t}{R_{ad1}} = 0.4632 \text{ A}$
 (labelled min) $E_a = 191.1510 \text{ V}$
 $k\phi_{max} = \frac{E_a}{w} = 1.5267$
 \vdots
 $E_{afL} = 276.4685 \text{ V}$
 $I_{afL} = 59.3775 \text{ A}$
 $w_{FL} = 181.0848 \text{ rad/s} \xrightarrow{\times \frac{60}{2\pi}} 1721.2902 \text{ rpm}$

IDLING SPEED: $P_{id} = P_{loss}$

Solve $P_{loss} = E_a I_a$
 $I_a = \frac{V_t - E_a}{R_a} = 2.6529 \text{ A}$
 $E_a = 282.7082 \text{ V}$
 $w_{min/max} = \frac{E_{min/max}}{k\phi_{min/max}} = 122.0176 / 185.1758$
 ↴ from previously ↓ ↓
 1165.9459 rpm 1708.1787 rpm

6)

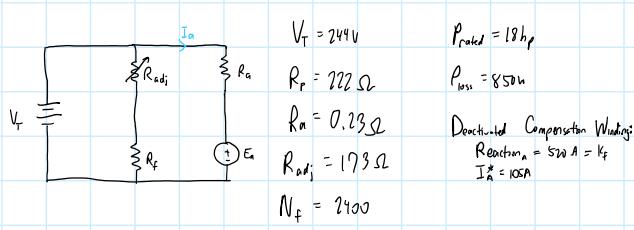

$$V_t = 244 \text{ V}$$
 $R_p = 222 \Omega$
 $R_a = 0.23 \Omega$
 $R_{ad1} = 193 \Omega$
 $N_f = 2400$

Deactivated Compensation Winding:
 $R_{ad2} = 520 \Omega = k_f$
 $I_f^* = 10 \text{ A}$

WL compensation

$$I_f = \frac{V_t}{R_{ad1} + R_p} = 0.6177 \text{ A}$$

$$E_a = 233.8861 \text{ V}$$

$$k\phi = \frac{E_a}{w} = 1.8612$$

$$P_{loss} + P_{rotated} = E_a \left(\frac{V_t - E_a}{R_a} \right)$$

$$E_{afL} = 229.7036 \text{ V} \quad I_{afL} = \frac{V_t - E_{afL}}{R_a} = 62.1584$$

$$w_{FL} = 123.4165 \text{ rad/s} \xrightarrow{\times \frac{60}{2\pi}} 1178.5409 \text{ rpm}$$

WB compensation

$$I_f^* = I_f - \frac{k_f I_{afL}}{N_f} = 0.4895 \text{ A}$$

$$E_a^* = 200.1565$$

$$k\phi^* = \frac{E_a^*}{w} = 1.5989$$


⋮

$$w_{FL}^* = \frac{E_a^*}{k\phi^*} = 107.9174 \text{ rad/s} \xrightarrow{\times \frac{60}{2\pi}} 1030.5352 \text{ rpm}$$

$$P_{loss} + P_{rotated} = E_a^* \left(\frac{V_t - k\phi^* w}{R_a} \right)$$

$$E_{afL}^* = \frac{P_{loss} + P_{rotated}}{I_f^*} = 135.9810 \text{ V}$$
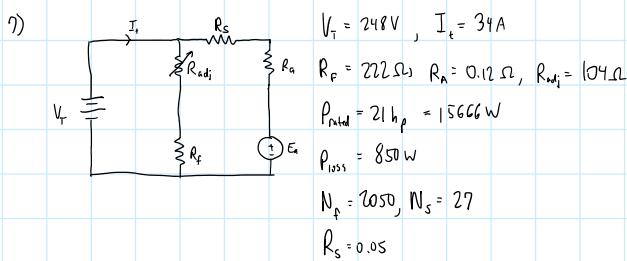
$$w_{FL}^* = 100.1831 \text{ rad/s} \xrightarrow{\times \frac{60}{2\pi}} 956.6795 \text{ rpm}$$



a) $I_t = I_f + I_a$

$$I_t = \frac{V_t}{R_f + R_{sd}} + I_a \rightarrow I_f = 0.7607 \text{ A}$$
 $\rightarrow I_a = 33.2393 \text{ A} \rightarrow E_a = 242.3493 \text{ V}$
 $I_f^* = I_f + \frac{N_s}{N_f} I_a = 1.1915 \text{ A} \xrightarrow{\text{LIP}} E_a^* = 287.9117 \text{ V}$

$\omega_{new} = 1200 \cdot \frac{E_a}{E_a^*} = 1009.8571 \text{ rpm}$

b) $P_{TOT} = P_{loss} + P_{rated}$


 $E_a I_a = T \omega_{new} + P_{loss}$
 $\omega_{new} = \frac{2\pi}{60} \text{ rad/s}$
 $\rightarrow T = 68.1362 \text{ Nm}$

c) $E_a I_a = P_{loss} + P_{rated}$; $I_a = \frac{V_t - E_a}{R_s + R_a}$

 $\rightarrow E_a = 236.1683 \text{ V} \rightarrow E_{a_{FL}}$
 $\rightarrow I_a = 69.9509 \text{ A}$
 $I_f = \frac{V_t}{R_{sd} + R_f} = 0.7607 \text{ A}$
 $I_t = I_f + I_a = 70.7117 \text{ A}$

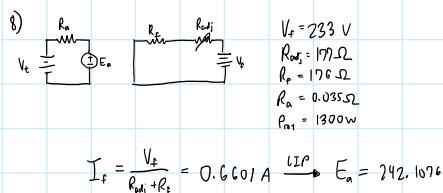d) $I_{fd} = \frac{N_f}{N_p} \frac{I_f + N_s I_a}{c} = 1.6870$

 $E_{a_{fd}} = 296.8671 \text{ V}$
 $\omega_{fd} = \frac{E_{a_{fd}}}{E_{a_{FL}}} \times 1200 = 954.4001 \text{ rpm}$



$I_f = \frac{V_t}{R_{sd} + R_f} = 0.6601 \text{ A} \xrightarrow{\text{LIP}} E_a = 242.1076$

a) $V_t = 280 \text{ V}$

 $P_{rated} = E_{a1} \left(\frac{V_t - E_{a1}}{R_a} \right) \rightarrow E_{a1} = 279.1374 \text{ V}$
 $\omega = 1389.0067 \text{ rpm}$

b) $V_t = 292 \text{ V} \rightarrow E_{a1} = 291.8441 \text{ V}$

 $\omega = 1446.5125 \text{ rpm}$

c) $V_t = 223 \text{ V} \rightarrow E_{a1} = 222.2958 \text{ V}$

 $\omega = 1104.2813 \text{ rpm}$

$$9) \quad 130 < V_t < 250 \quad R_a = 0.29 \Omega$$

$$V_t = 210 \text{ V} \quad P_{rot} = 240 \text{ W}$$

$$97 < R_{adj} < 279$$

$$R_f = 278$$

$$\text{a) Max RPM: } V_t = 250, R_{adj} = 279 \Omega$$

$$I_f = \frac{V_t}{R_f + R_{adj}} = 0.4158 \text{ A} \xrightarrow{\text{Lip}} E_a = 175.6328 \text{ V}$$

$$P_{rot} = E_{ai} \left(\frac{V_t - E_a}{R_a} \right) \rightarrow E_{ai} = 249.9213 \text{ V}$$

$$W_{max} = f \cdot \frac{E_{ai}}{E_a} = 1706.7049 \text{ RPM}$$

$$\text{b) Min RPM: } V_t = 130, R_{adj} = 97 \Omega$$

$$I_f = \frac{V_t}{R_f + R_{adj}} = 0.3162 \text{ A} \xrightarrow{\text{Lip}} E_a = 239.4079 \text{ V}$$

$$P_{rot} = E_{ai} \left(\frac{V_t - E_a}{R_a} \right) \rightarrow E_{ai} = 129.4624 \text{ V}$$

$$W_{min} = f \cdot \frac{E_{ai}}{E_a} = 648.9135 \text{ RPM}$$

$$10) \quad V_t = 276 \text{ V}, I_t = 43 \text{ A}, N = 31, R_s = 0.04 \Omega, R_a = 0.04 \Omega, f = 900 \text{ RPM}$$

a,b)

$$V_t = E_a + I_a (R_s + R_a) \rightarrow E_a = 274.78 \text{ V}$$

$$I_a = \frac{I_t}{2} = 21.5 \text{ A}$$

$$MMF_a = N \cdot I_a = 666.5 \xrightarrow{\text{Lip}} E_{af} = 113.315 = k\phi_w$$

$$k\phi = \frac{E_{af}}{w} = E_{af} \cdot \frac{60}{2\pi f} = 1.2023$$

$$T_{50\%} = k\phi I_a = 25.8497 \text{ Nm}$$

$$W_{50\%} = f \cdot \frac{E_a}{E_{af}} = 2198.4583 \text{ RPM}$$

$$\begin{aligned} E_a &= V_t - I_a (R_a + R_s) \\ I_a &= \frac{I_t}{2} = \frac{43}{2} \\ MMF_a &= N I_a \dots \end{aligned}$$

$$\rightarrow E_{af}$$

$$w = f \left(\frac{E_{af}}{E_a} \right)$$

$$T = k\phi I_a$$

$$c,d) \quad I_a = I_t$$

$$V_t = E_a + I_a (R_s + R_a) \rightarrow E_a = 272.56 \text{ V}$$

$$MMF_b = N \cdot I_a = 133 \xrightarrow{\text{Lip}} E_{af_b} = 175.308 \text{ V}$$

$$k\phi = \frac{E_{af_b}}{w} = 1.1601$$

$$T_{100\%} = k\phi I_a = 79.9833 \text{ Nm}$$

$$W_{100\%} = f \cdot \frac{E_a}{E_{af_b}} = 1399.2714 \text{ RPM}$$

$$11) \quad V_t = 265 \text{ V}, f = 720 \text{ rpm}, w = 1620 \text{ rpm}, R_a = 0.36 \Omega, I_f = 1.4 \text{ A}, I_t = 11.75 \text{ A}$$

$$I_{f,new} = 1.1 \text{ A}$$

$$I_a = I_t - I_f = 9.85 \text{ A}$$

$$E_a = V_t - I_a R_a = 261.454 \text{ V}$$

$$I_{a_2} = \frac{V_t}{\left(\frac{I_{f,new}}{I_f} \right)^2 (R_a)} = 15.8241 \text{ A}$$

$$E_{a_2} = V_t - I_{a_2} R_a = 259.3033 \text{ V}$$

$$w_2 = w \left(\frac{E_{a_2}}{E_a} \right) \left(\frac{I_f}{I_{f,new}} \right) = 1514.7046 \text{ RPM}$$

$$I_{L2} = I_{a_2} + I_{f,new} = 16.944 \text{ A}$$

$$P_{mech} = E_{a_2} I_{a_2} = 4103.2481 \text{ W}$$

$$\eta = \frac{P_{mech}}{V_t I_{L2}} \times 100\% = 91.4904\%$$

$$12) \quad T = 295 \text{ Nm}, \quad V_T = 570V, \quad w = 1260 rpm, \quad r_a = 0.35 \Omega$$

$$\begin{aligned} \text{a) } P &= \frac{2\pi f W}{60} T \\ &= 1155 \pi \end{aligned}$$

$$\text{b) } \tilde{I}_2 = \tilde{I}_1 \\ \Phi_1 I_{a_1} = \Phi_2 I_{a_2} \\ \Phi_2 = (1 - 0.29) \Phi_1 = 0.71 \Phi_1 \\ I_{a_2} = \frac{\Phi_1}{0.71 \Phi_1} I_{a_1} = \underline{93.4688 \text{ A}}$$

$$\frac{E_{n_1}}{E_{n_2}} = \frac{\phi_1}{\phi_2} \frac{W}{W_2}$$

$$E_{n_2} = V_t - I_{n_2} R_a = 537.2859 V$$

$$I_{n_1} = \frac{P}{E_{n_1}} = 546.7730 V$$

$$13) \quad V_t = 180V, \quad P = 5.8 \text{ kW}, \quad \omega = 2100 \text{ rpm}, \quad E_a = 13V$$

$$\text{a) } I_{a_F} = \frac{P}{V_a - E_a} = 34.7305 \text{ A}$$

$$R_a = \frac{E_a}{I_{a_F}} = 0.3943 \text{ } \Omega$$

$$I_a^* = \frac{V_a}{R_a} = 480.8844 \text{ A}$$

$$R_s = \frac{V_t}{1.5 I_{a_{FL}}} - R_a = 3.0809$$

$$c) k\phi = \frac{V_a - E_a}{\omega - \frac{E_a}{60}} = 0.7594$$

$$W_2 = \frac{V_a}{(1 - \frac{\phi}{60})} = 191.1946 \text{ rad/s} \xrightarrow{\times \frac{60}{2.71}} 1833.4132 \text{ rpm}$$

given

$$14) V_t = 150 \text{ V}, I_a = 15 \text{ A}, W = 2100 \text{ rpm}, R_a = 0.22 \Omega, \phi_2 = 0.075 \phi_1$$

$$\rightarrow I_f = 0$$

$$E_{bl} = V_t - I_a R_a = 146.7 \text{ V}$$

$$\frac{E_{b2}}{E_{b1}} = \frac{\phi_2}{\phi_1} \quad \text{from } E_b = k\phi_w$$

$$\rightarrow E_{b2} = 11.6675V$$

$$I_{a2} = \frac{V_t - E_{b2}}{R_a} = 31.8068A$$

$$\frac{E_{b2}}{E_{b1}} = \frac{\phi_2}{\phi_1} \cdot \frac{N_2}{N_1}$$

CPM

speed

$k\phi = \frac{E_{b1}}{W \times \frac{2\pi}{60}} = 0.6671$

$k\phi^* = k\phi \times 0.075 = 0.05$

$T = k\phi i_a = 10.0063 \text{ Nm}$

$\tilde{T} = k\phi^* \left(\frac{V_1 - k\phi^* w_2}{\rho} \right) \rightarrow$

$$15) \quad V_L = 640V, R_L = 0.34\Omega, \overbrace{R_f + R_{L'}}^{R_f^*} = 435\Omega$$

$$I_m = 100A, \omega_1 = 1750 \text{ rpm}, \omega_2 = 1050 \text{ rpm}$$

$$\overline{I}_{f_1} = \frac{V_T}{R_{f_1}^x} = 1.4713 \text{ A}$$

$$I_{f_1} = \frac{V_T}{R_f} = 1.4913 \text{ A}$$

$$I_{a_1} = I_m - I_{f_1} = 98.5187 \text{ A}$$

$$E_{a_1} + V_T - I_{a_1} R_a = 606.5002 \text{ V}$$

$$I_{f_1} = I_{f_1}$$

$$I_{a_1} = I_{a_1} \cdot \frac{\omega_2}{\omega_1} = 82.7641$$

$$R_{ada} = \left(\left(\frac{\omega_2}{\omega_1} E_{a_1} - V_T \right) \left(-\frac{1}{I_{a_1}} \right) - R_a \right) = 1.1393 \Omega$$