


1. Transmission Lines

Tuesday, September 5, 2023 9:18 PM


1.1) Wave Properties and Mathematical Formulation

What is a Wave?

- A transfer of energy

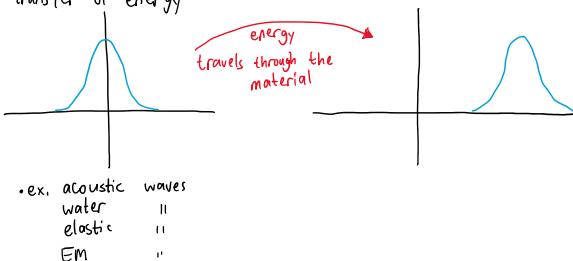

Basic Idea: Translation

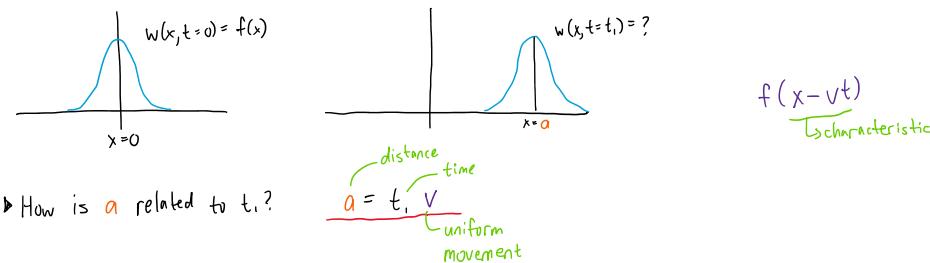

Q1 In the video describing wave translation, the wave pulse, $f(x)$, has a peak at $x=0$ when $t=0$. The pulse moves uniformly with velocity v to a new position where the peak is now at $x=a$ when $t=t_1$. (ie. $a = vt_1$)

$$f(x+a) = f(x+vt_1)$$

$$f(x)$$

> $f(x-a) = f(x-vt_1)$ at $x=a$, $f(x-a) = f(a-a) = f(0)$ is the peak of the pulse

Q2 We have just found that a wave traveling at uniform speed, v , will cover a distance d in time t given by the formula $d=vt$. let's apply this to where we live in Vancouver, an earthquake-prone zone. An earthquake is an elastic wave giving rise to two waves: a compressional wave and a shear wave

Parameters we will need:


- 1) Distance from Vancouver to the epicenter, d , is 420 km
- 2) Compression wave velocity, v_p , is 7 km/s
- 3) The shear wave velocity, v_s , is 3 km/s

What is the time difference (in seconds) between the arrival of the compression and shear waves in Vancouver?

80

Basic Wave Properties — Waves and Phase Velocity

Sine Waves (two snapshots)

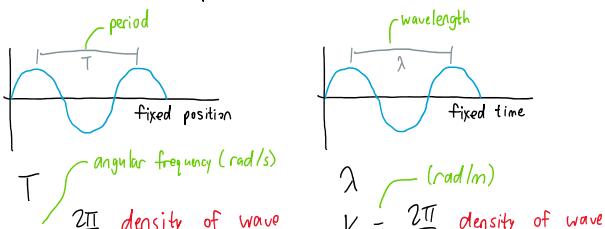

$$\omega = \frac{2\pi}{T} \text{ angular frequency (rad/s)}$$

density of wave per distance

$$\lambda = \frac{2\pi}{\omega} \text{ (rad/m)}$$

(rad/m)

$$K = \frac{2\pi}{\lambda} \text{ density of wave per time}$$

$$V = f\lambda \quad (\text{phase velocity})$$

$$= (2\pi f) \frac{\lambda}{2\pi}$$

$$= \omega \frac{1}{\frac{2\pi}{\lambda}} k$$

$$V = \frac{\omega}{K} \frac{\text{rad/s}}{\text{rad/m}} \quad \text{velocity of a point on a wave}$$

Q We have previously shown that a wave traveling to the right along the x-axis, in the direction of increasing positive x, can be described by the function $f(x-vt)$ where V is the wavespeed or phase velocity in one dimension, x is the spatial wave location, t is the time, and f is the pulse shape. Let's assume that our wave has the shape of a cosine (periodic). We also know for a periodic wave that $V_{\text{phase}} = \frac{\omega}{K}$. Making these substitutions, our wave becomes $\cos(kx - \omega t)$.

The phase velocity of this wave is:

$$V_{\text{phase}} = \frac{k}{\omega}$$

Indeterminate

$$V_{\text{phase}} = \frac{\omega}{K}$$

$$V_{\text{phase}} = \frac{\omega^2}{K^2}$$

Basic Wave Properties - Group Velocity

- attenuation Wave amplitude decreases as the wave goes through the material
- reflection & refraction
- dispersion & group velocity a bunch of frequencies mixed together in a packet and look at how the speed of the packet moves
- diffraction enhanced form of light scattering and bending. Has to do with shadows

Group Velocity

$$A(x,t) = \cos[(K + \delta K)x - (\omega + \delta\omega)t] + \cos[(K - \delta K)x - (\omega - \delta\omega)t] \quad \delta\omega \ll \omega$$

$$= 2 \cos(Kx - \omega t) \cos(\delta Kx - \delta\omega t)$$



$$V_p = \frac{C}{n(\omega)} = \frac{\omega}{K}$$

prism
speed of light
index of refraction

$$\frac{d\omega}{dk} \stackrel{?}{=}$$

$$K = \frac{\omega n(\omega)}{C}$$

If we can calculate this, we can easily get $\frac{d\omega}{dk}$

Simple Case

$$\omega = V_p K$$

$$\frac{d\omega}{dk} = V_p$$

phase

$$\frac{d\omega}{dk} = \left(\frac{dK}{d\omega} \right)^{-1} = \left(\frac{1}{C} \left[n(\omega) + \omega \frac{dn}{d\omega} \right] \right)^{-1} = \frac{C}{n(\omega) + \omega \frac{dn}{d\omega}}$$

group velocity of light waves going to the prism

in some books, known as $\frac{C}{n_g}$

Q Suppose we have two waves of the cosine type, with frequencies $\omega + \delta\omega$ and $\omega - \delta\omega$ where $\delta\omega \ll \omega$. The corresponding wave numbers will be

Q1 Suppose we have two waves of the cosine type, with frequencies $\omega + \delta\omega$ and $\omega - \delta\omega$ where $\delta\omega \ll \omega$. The corresponding wave numbers will be $k + \delta k$ and $k - \delta k$. The sum of our two waves, $A(x,t)$ is given by $A(x,t) = \cos[(k + \delta k)x - (\omega + \delta\omega)t] + \cos[(k - \delta k)x - (\omega - \delta\omega)t]$

$A(x,t)$ can be written as:

$$2 \cos(kx + \omega t) \cos(\delta kx + \delta \omega t)$$

$$2 \cos(kx - \omega t) \cos(\delta kx + \delta \omega t)$$

> $2 \cos(kx - \omega t) \cos(\delta kx - \delta \omega t)$ Using trig identity $\cos(C) + \cos(D) = 2 \cos\left(\frac{(C+D)}{2}\right) \cos\left(\frac{(C-D)}{2}\right)$

$$2 \cos(kx + \omega t) \cos(\delta kx - \delta \omega t)$$

Q2 Conditions: $\delta k \ll k$ and $\delta\omega \ll \omega$

In the interpretation of the results of the previous question on "close" sinusoids, the final results may be interpreted as a

> rapidly oscillating wave with a slowly varying modulation envelope

The rapid oscillation will have frequency ω while the slowly varying oscillation will have frequency $\delta\omega$

rapidly oscillating wave with a rapidly varying modulation envelope


slowly oscillating wave with a slowly varying modulation envelope

slowly oscillating wave with a rapidly varying modulation envelope

1.2) Modelling Lossless Transmission Lines

Motivation for Differentiation of the Wave Description

$f(x-vt)$ ← Model for Waves

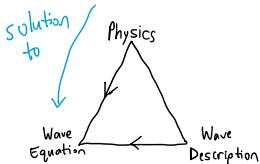

Differentiating the Wave Description

Forward waves $\rightarrow f(x-vt)$

Physics: $V(x,t) = V^+ f(x-vt)$ Voltage

$$\begin{aligned} I(x,t) &= I^+ f(x-vt) \\ &= \frac{V^+}{Z} f(x-vt) \end{aligned}$$

$$V(x,t) = V^+ f(x-vt) = V^+ f(\eta(x,t)) \quad \eta(x,t) = x - vt$$

$$\frac{\partial \eta}{\partial x} = 1 \quad \frac{\partial \eta}{\partial t} = -v$$

$$\frac{\partial V}{\partial x} = V^+ \frac{df}{d\eta} \frac{d\eta}{dx} = V^+ \frac{df}{d\eta} \cdot 1$$

$$\frac{\partial V}{\partial t} = V^+ \frac{df}{d\eta} \frac{d\eta}{dt} = V^+ \frac{df}{d\eta} \cdot (-v) = \frac{\partial V}{\partial x} (-v)$$

$$\frac{\partial V}{\partial t} = -v \frac{\partial V}{\partial x} \rightarrow \frac{\partial V}{\partial x} + \frac{1}{v} \frac{\partial V}{\partial t} = 0 \quad \text{Wave travelling to the right in 1D}$$

- Wave travelling to the left

Q1 Consider a wave described by $f(x+vt)$ where v is a positive number. As t increases, the wave travels in the direction of

> decreasing x

increasing x

> decreasing x

increasing x

$x=1$

both increasing and decreasing x

Q2 Let us denote the derivative of $f(x+vt)$ with respect to the argument $x+vt$ by f' (i.e. $f' = \frac{df}{d(x+vt)}$). When we differentiate $f(x+vt)$ with respect to t , we obtain the result

> $v f'$

$-v f'$

$-v f(x+vt)$

$v(f')$

Q3 Suppose $V(z, t) = V^+ g(\alpha(t - \frac{z}{v}))$ where g = Some function of wave, α = constant, v = velocity, z = distance that the wave travels down the transmission line, and V^+ = voltage amplitude constant

$V(z, t)$ satisfies the equation given by :

$$\frac{\partial V}{\partial z} + \frac{\alpha}{v} \frac{\partial V}{\partial t} = 0$$

$$\frac{\partial V}{\partial z} + \frac{1}{v} \frac{\partial V}{\partial t} = 0$$

$$\frac{\partial V}{\partial z} \frac{\partial z}{\partial t} + \frac{\alpha}{v} \frac{\partial V}{\partial t} \frac{\partial t}{\partial z} = 0$$

$$\frac{\partial V}{\partial t} + \frac{1}{v} \frac{\partial V}{\partial z} = 0$$

$$\eta(x, t) = \alpha t - \frac{\alpha x}{v}$$


$$\frac{\partial \eta}{\partial x} = \frac{\alpha}{v} \quad \frac{\partial \eta}{\partial t} = \alpha$$

$$\frac{\partial V}{\partial x} = V^+ g \frac{\partial f}{\partial \eta} \frac{\partial \eta}{\partial x} = V^+ g \frac{\partial f}{\partial \eta} \frac{\alpha}{v}$$


$$\frac{\partial V}{\partial t} = V^+ g \frac{\partial f}{\partial \eta} \frac{\partial \eta}{\partial t} = V^+ g \frac{\partial f}{\partial \eta} \alpha$$

$$\rightarrow \frac{\partial V}{\partial x} = \frac{\partial V}{\partial t} \cdot \frac{-1}{V} \rightarrow \frac{\partial V}{\partial x} + \frac{1}{v} \frac{\partial V}{\partial t} = 0$$

Lossless Transmission Line Model

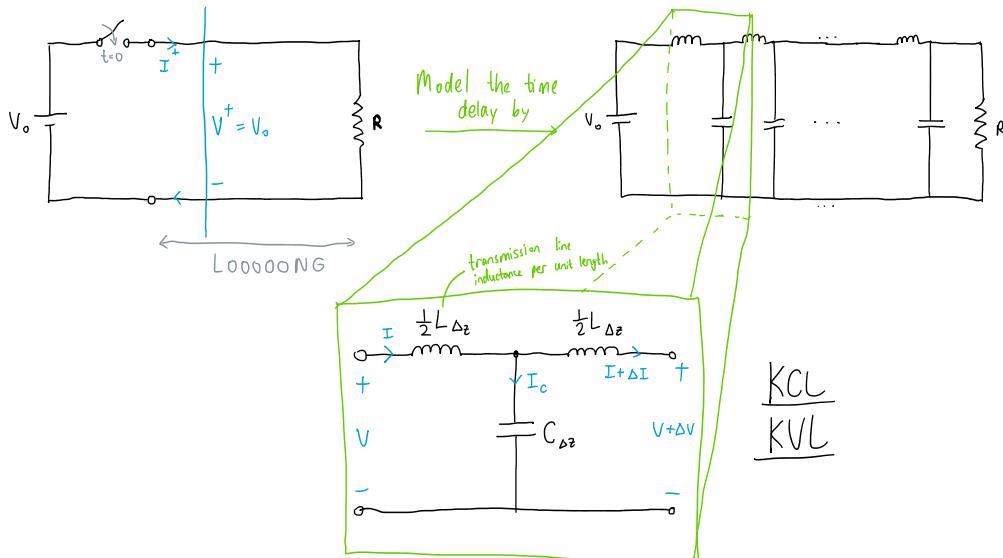

KVL and KCL on Lossless Model

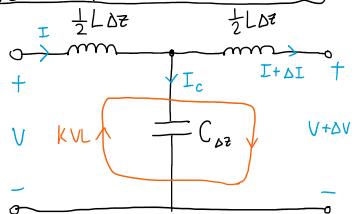

$$KVL: V - \frac{1}{2} L \Delta z \frac{\partial I}{\partial t} - \frac{1}{2} L \Delta z \frac{\partial}{\partial t} (I + \Delta I) - (V + \Delta V) = 0$$
$$\therefore \frac{\partial I}{\partial t} (I + \Delta I) = - \Delta V$$

$$\text{KVL: } V - \frac{1}{2} L \Delta z \frac{\partial I}{\partial t} - \frac{1}{2} L \Delta z \frac{\partial}{\partial t} (I + \Delta I) - (V + \Delta V) = 0$$

$$L \Delta z \frac{\partial I}{\partial t} (1 + \Delta I)^0 = -\Delta V$$

$$\frac{\Delta V}{\Delta z} = -L \frac{\partial I}{\partial t}$$

$$\boxed{\frac{\partial V}{\partial z} = -L \frac{\partial I}{\partial t}}$$

$$\text{KCL: } I = I_c + \Delta I$$

$$\cancel{I} = C \Delta z \frac{\partial v}{\partial t} + \cancel{I} + \Delta I$$

$$\frac{\Delta I}{\Delta z} = -C \frac{\partial v}{\partial t}$$

$$\boxed{\frac{\partial I}{\partial z} = -C \frac{\partial v}{\partial t}}$$

Q1 Which of the following is true?

> Waves traveling down a transmission line have a maximum speed limit

The transmission line model presented in this video with lumped L and C elements dissipate power as voltage and current waves pass through

A transmission line described by the lumped element model only supports waves traveling in one direction

Q2 Is the statement true: "A wave is launched down a transmission line when a battery is switched on."

It depends on the battery voltage, yes if it is higher than 5V

> Yes

No

Q3 Under which of the following scenario(s) is/are the lossless transmission line model applicable for modeling the transmission line?


> Modeling a 100m long lossless transmission line terminated by a 50Ω resistive load

> Modeling a 100m long lossless transmission line terminated by an open circuit

> Modeling a 100m long lossless transmission line terminated by a short circuit

> Modeling an infinitely long lossless transmission line

The Chain Rule

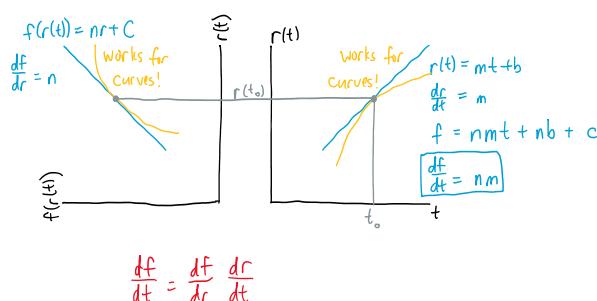

1.3) Simple Waves on Transmission Lines

Intuition for 1st and 2nd Order Wave Equations


1st order right-travelling wave: $\frac{\partial v}{\partial x} + \frac{1}{v} \frac{\partial v}{\partial t} = 0$ ←

left-travelling wave: $\frac{\partial v}{\partial x} - \frac{1}{v} \frac{\partial v}{\partial t} = 0$ ←

Intuition for 1st and 2nd Order Wave Equations


1st order right-travelling wave: $\frac{\partial v}{\partial x} + \frac{1}{v} \frac{\partial v}{\partial t} = 0$ ←
 left-travelling wave: $\frac{\partial v}{\partial x} - \frac{1}{v} \frac{\partial v}{\partial t} = 0$ ←

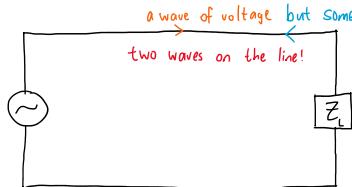2nd order: $\frac{\partial^2 v}{\partial x^2} - \frac{1}{v^2} \frac{\partial^2 v}{\partial t^2} = 0$



a wave of voltage but sometimes, when the wave hits the load, the load appears "stiff" to the wave.
 So we get a reflection back.

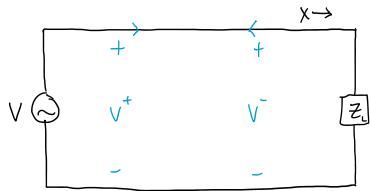
Since we have two first-order equations here, it will lead us to that 2nd order equation previously.



$$V(x,t) = V^+ f(x-vt) + V^- f(x+vt)$$

$$\frac{\partial^2 v}{\partial x^2} - \frac{1}{v^2} \frac{\partial^2 v}{\partial t^2} = 0$$

Slinky Waves

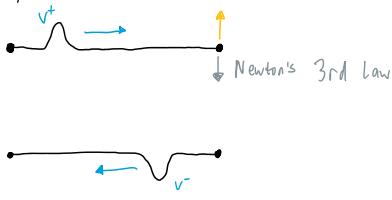

Simple Waves on Transmission Lines — Voltage Waves

$$\text{KVL: } \frac{\partial V}{\partial z} = -L \frac{\partial I}{\partial t} \quad \rightarrow \quad \frac{\partial^2 V}{\partial z^2} = -L \frac{\partial^2 I}{\partial t \partial z}$$

$$\text{KCL: } \frac{\partial I}{\partial z} = -C \frac{\partial V}{\partial t} \quad \rightarrow \quad \frac{\partial I}{\partial t \partial z} = -C \frac{\partial^2 V}{\partial t^2}$$

$$\begin{aligned} \frac{\partial^2 V}{\partial z^2} &= \frac{1}{v^2} \frac{\partial^2 V}{\partial t^2} \\ \frac{\partial^2 V}{\partial z^2} &= [LC] \frac{\partial^2 V}{\partial t^2} \\ [LC] &= \frac{HF}{m^2} \\ V &= \frac{1}{\sqrt{LC}} \end{aligned}$$

velocity
Volts
time

Simple Voltage and Current Waves on Lossless Lines

$$\frac{\partial^2 V}{\partial z^2} = \frac{1}{v^2} \frac{\partial^2 V}{\partial t^2} \rightarrow V(z,t) = f_1(t - \frac{z}{v}) + f_2(t + \frac{z}{v})$$

forward backward

$$\frac{\partial I}{\partial t} = -\frac{1}{L} \frac{\partial V}{\partial z}$$

$$\frac{\partial I}{\partial t} = -\frac{1}{L} \frac{\partial}{\partial z} [f_1(t - \frac{z}{v}) + f_2(t + \frac{z}{v})]$$

$$I(z,t) = \frac{1}{Lv} [f_1(t - \frac{z}{v}) - f_2(t + \frac{z}{v})]$$

$$\eta_1(z,t) = t - \frac{z}{v}$$

$$\eta_2(z,t) = t + \frac{z}{v}$$

$$\frac{\partial \eta_1}{\partial z} = -\frac{1}{v} \quad \frac{\partial \eta_1}{\partial t} = 1$$

$$\frac{\partial \eta_2}{\partial z} = \frac{1}{v} \quad \frac{\partial \eta_2}{\partial t} = 1$$

$$\rightarrow \frac{\partial I}{\partial t} = -\frac{1}{L} \left(\frac{\partial f_1}{\partial \eta_1} \frac{\partial \eta_1}{\partial z} + \frac{\partial f_2}{\partial \eta_2} \frac{\partial \eta_2}{\partial z} \right)$$

$$= -\frac{1}{L} \left(\frac{\partial f_1}{\partial \eta_1} \left(-\frac{1}{v} \right) + \frac{\partial f_2}{\partial \eta_2} \right)$$

$$\int \frac{\partial I}{\partial t} = \int \left(\frac{1}{Lv} \left(\frac{\partial f_1}{\partial \eta_1} - \frac{\partial f_2}{\partial \eta_2} \right) \right)$$

$$I(z,t) = \frac{1}{Lv} \left(f_1(t - \frac{z}{v}) - f_2(t + \frac{z}{v}) \right) = I^+ + I^-$$

$$\frac{\partial I}{\partial z} + \frac{1}{v} \frac{\partial f}{\partial t} = 0$$

$$I^+ f = 0$$

$$I^+ = \frac{1}{v} \frac{\partial f}{\partial t}$$

$$I^+ V = I^+ f(z - vt) + I^+ g(z + vt)$$

$$I^- a = 0$$

one-wave wave equation

$$I(z,t) = \frac{1}{L} \left(f_1(t - \frac{z}{v}) - f_2(t + \frac{z}{v}) \right) = I^+ + I^-$$

$$L^+ V = L^+ f(z-vt) + L^+ g(z+vt) \quad \text{one-wave wave equation}$$

$$L^- g = 0$$

$$L^- = \frac{\partial}{\partial z} - \frac{1}{v} \frac{\partial}{\partial t}$$


$$L^- L^+ V = 0 + L^- L^+ g(z+vt)$$

$$L^- L^+ V = 0 + L^+ L^- g(z+vt)$$

$$L^- L^+ V = 0 \quad L^- L^+ = \frac{\partial^2}{\partial z^2} - \frac{1}{v^2} \frac{\partial^2}{\partial t^2}$$

$$L^- L^+ V = \left[\frac{\partial^2}{\partial z^2} - \frac{1}{v^2} \frac{\partial^2}{\partial t^2} \right] V = 0$$


Intuition of Backward Current Sign Flip

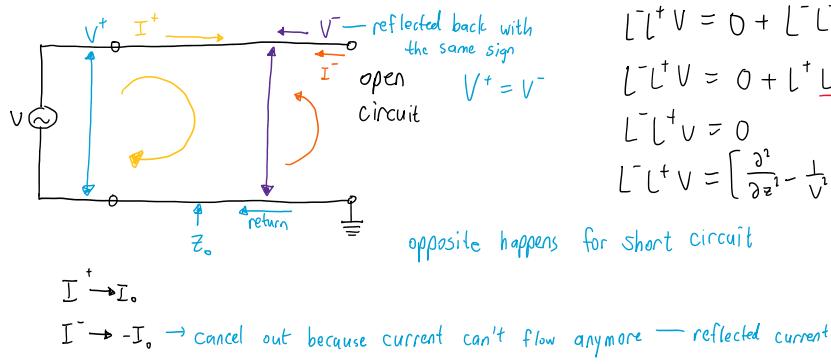

Q On the transmission line,

- > the polarity of the backward current, I^- , is the reverse of the polarity of the backward voltage, V^-
- > the polarity of the backward current, I^- , is the same of the polarity of the forward voltage, V^+
- > the polarity of the backward current, I^- , is the same of the polarity of the forward current, I^+
- > the polarity of the forward current, I^+ , is the reverse of the polarity of the forward voltage, V^+

Voltage Functions and Notations

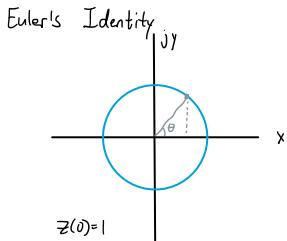

$$\begin{aligned} x + jy &= z \\ z &= \cos \theta + j \sin \theta \\ \frac{dz}{d\theta} &= -\sin \theta + j \cos \theta \\ &= j(j \sin \theta + \cos \theta) \\ \frac{dz}{d\theta} &= jz \\ \frac{dz}{z} &= j d\theta \rightarrow \ln z = j\theta + C \\ e^{\ln z} &= z = e^{j\theta+C} = e^C e^{j\theta} \\ z(0) &= 1 = e^C \\ z &= e^{j\theta} \end{aligned}$$

Voltage Function & Notations

$$V^+ = f_1 \left(t - \frac{z}{v} \right)$$

$f = \text{cosine exp.}$

$$V(z, t) = \frac{1}{2} \left(N_d e^{j\theta} \right) e^{\pm j\beta z} e^{j\omega t} + \beta^*$$

$$V_c(z, t) = V_o e^{\pm j\beta z} e^{j\omega t}$$

$$V_s(z, t) = V_o e^{\pm j\beta z}$$

$$\begin{aligned} \cos(x) &= \frac{e^{ix} + e^{-ix}}{2j} \\ &= \frac{e^{jx} - e^{-jx}}{2j} \\ &= \frac{e^{jx} - e^{-jx}}{2j} \end{aligned}$$

$$\begin{aligned} & \frac{e^{jx} - e^{-jx}}{2j} \\ & \frac{2j}{2} \\ & \cancel{\frac{e^{jx} - e^{-jx}}{2}} \\ & \cancel{\frac{e^{jx} + e^{-jx}}{2}} \end{aligned}$$

Q2 In the complex voltage representation $V_c(z, t) = V_0 e^{+j\beta z} e^{j\omega t}$, what are the units of:

ω

- > rad/s
- rad/m
- V

β

- rad/s
- > rad/m
- V

1.4) Lossy Transmission Lines and Phasor Representation

Energy Flow in Transmission Line via TEM Waves

TEM for T (transmission) Lines

transverse electro-magnetic waves

voltage $V(z, t) = f_1(t - \frac{z}{v}) + f_2(t + \frac{z}{v})$ to make things simple


current $I(z, t) = \frac{1}{Z_0} \{ f_1(t - \frac{z}{v}) - f_2(t + \frac{z}{v}) \}$

forward I^+ backward I^-

velocity $v = \frac{1}{\mu C}$

characteristic impedance $Z_0 = \sqrt{\frac{\mu}{C}} = Lv$

We want to visualize this.

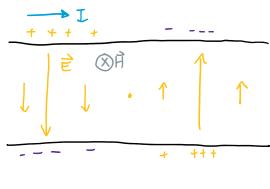


$$[\vec{E}] = \frac{V}{m}$$

$$[\vec{H}] = \frac{A}{m}$$

Each line in the xy plane is perpendicular/transverse to the direction of the current and transverse to the direction of the energy flow.

Full Transmission Line Model

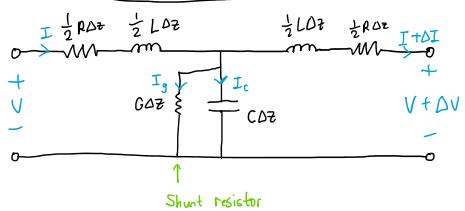

KVL: $\frac{\partial V}{\partial z} = -(IR + L \frac{\partial I}{\partial t})$

KCL: $\frac{\partial I}{\partial z} = -(GV + C \frac{\partial V}{\partial t})$

Q The following losses are modeled by the series resistance R :

- > electrical resistance in the conductors

current leakage through the dielectric between conductors (dielectric loss)

capacitive charging loss

- > magnetic field switch losses (often insignificant)

Phasor Solutions

Assume that all time variation is of the solution dependent on $e^{j\omega t}$.

So all first time derivatives will be replaced by $j\omega e^{j\omega t}$ and second time derivatives will be replaced by $-\omega^2 e^{j\omega t}$

- Assume that all time variation is of the solution dependent on $e^{j\omega t}$.

So all first time derivatives will be replaced by $j\omega e^{j\omega t}$ and second time derivatives will be replaced by $-\omega^2 e^{j\omega t}$

- Previously:

$$\frac{\partial V}{\partial z} = -(RI + L \frac{\partial I}{\partial t})$$

$$\frac{\partial I}{\partial z} = -(GV + C \frac{\partial V}{\partial t})$$

- Combining this we get one voltage equation:

$$\frac{d^2V}{dz^2} = LC \frac{d^2V}{dt^2} + (LG + RC) \frac{\partial V}{\partial t} + RGV$$

If there was no damping, resistance, conductance in the system, then last two terms would disappear

- Assuming the phasor time dependence we end up with the phasor expression

$$\frac{d^2V_s}{dz^2} = -\omega^2 LCV_s + j\omega(LG + RC)V_s + RGV_s$$

- We can regroup the RHS of the previous equation to get

$$\frac{d^2V_s}{dz^2} = \underbrace{(R + j\omega L)}_Z \underbrace{(G + j\omega C)}_Y V_s = \gamma^2 V_s$$

\rightarrow Wave number

- Here $\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} = \sqrt{ZY} = \alpha + j\beta$ if there is no resistance R or conductance G , then α and β is K
whose solution is $V_s = \underbrace{V_o^+ e^{-\gamma z}}_{\text{Wave going towards the wall}} + \underbrace{V_o^- e^{\gamma z}}_{\text{Wave reflected back}}$ (as seen at the very top of the page)

and for current, we can follow analogous procedures to get

$$I_s = \underbrace{I_o^+ e^{-\gamma z}}_{\text{Same as for } V_s} + \underbrace{I_o^- e^{\gamma z}}$$

- We can apply similar methods to the first equations that we obtained using KVL & KCL, obtaining

$$\frac{dV_s}{dz} = -(R + j\omega L) I_s = -Z I_s \quad \text{eq} \leftarrow$$

and

$$\frac{dI_s}{dz} = -(G + j\omega C) V_s = -Y V_s$$

- Now substitute voltage and current solutions into to get

$$-\gamma V_o^+ e^{-\gamma z} + \gamma V_o^- e^{\gamma z} + \gamma V_o^- e^{\gamma z} = -Z(I_o^+ e^{-\gamma z} + I_o^- e^{\gamma z})$$

$$-\gamma V_o^+ = -Z I_o^+$$

$$\frac{V_o^+}{I_o^+} = \frac{Z}{\gamma} \rightarrow Z, \text{ Characteristic Impedance}$$

- We look at the forward & backward waves and match and we get the characteristic impedance as

$Z_0 = \text{transmission line voltage to current ratio at same position}$

$$= \frac{V_o^+}{I_o^+} = -\frac{V_o^-}{I_o^-} = \frac{Z}{\gamma} = \frac{Z}{\sqrt{ZY}} = \sqrt{\frac{Z}{Y}}$$

- Using the previous results for Z and Y we have the explicit expression

$$Z_0 = \sqrt{\frac{(R + j\omega L)}{(G + j\omega C)}} = |Z_0| e^{j\theta}$$

From the video, we have obtained $\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} = \sqrt{ZY} = \alpha + j\beta$

Considering the forward component of the phasor voltage, we have: $V_s^+ + V_o^+ e^{-(\alpha + j\beta)z} = V_o^+ e^{-\alpha z} e^{-j\beta z}$

Q1 From the mathematical intuition, $e^{-\alpha z}$ is ...

the oscillation (rotation of the phasor)

> the loss (exponential decay)

Q2 And $e^{-j\beta z}$ is ...

> the oscillation (rotation of the phasor)

the loss (exponential decay)

Q3 Here, we have introduced the characteristic impedance $Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}}$. Is the following statement true:

"When $R=0$ and $G=0$, Z_0 is always imaginary"

True

> False When $R=0, G=0$, $Z_0 = \sqrt{\frac{0+j\omega L}{0+j\omega C}} = \sqrt{\frac{L}{C}}$ which is purely real

Intuition of Characteristic Impedance



$$V = V_o e^{-\gamma z}$$




$$I = I_o e^{-\gamma z} = \frac{V_o^+}{Z_0^+} e^{-\gamma z} = \frac{V_o^+}{L/C} e^{-\gamma z} = \frac{V_o^+}{L \cdot \frac{1}{C}} e^{-\gamma z} = \frac{V_o}{\sqrt{LC}} e^{-\gamma z}$$

Locusless line

$$\gamma = \alpha + j\beta \rightarrow \alpha = 0, \gamma = j\beta$$

(for the case)

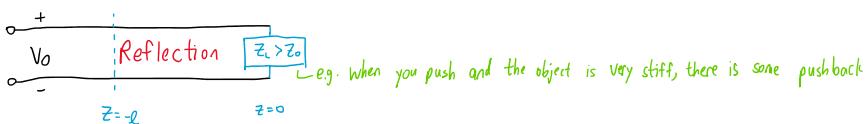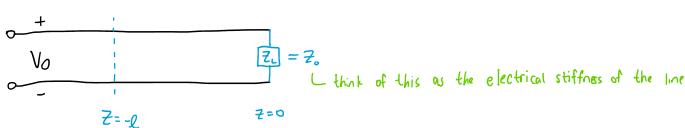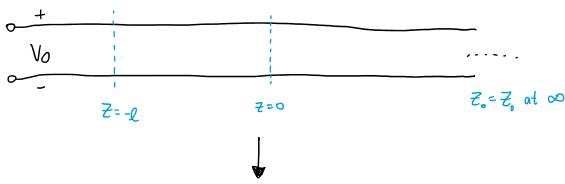Ratio of $\frac{V}{I} = \frac{V_o e^{-\gamma z}}{\frac{V_o}{Z_0} e^{-\gamma z}} = Z_0 \rightarrow$ constant along the line




Q Given that a voltage wave $V_s = (5V) e^{-j\beta z}$ enters an infinitely long transmission line with characteristic impedance $\tau = \sqrt{\frac{L}{C}} = \sqrt{\frac{1}{100}} = 0.1 \Omega$

Q Given that a voltage wave $V_s = (5V) e^{-j\beta z}$ enters an infinitely long transmission line with characteristic impedance $Z_0 = 50 \Omega$, what is the corresponding current amplitude I_s in $I_s = I_o e^{-j\beta z}$?
 $I_o = 0.1 \text{ A} \quad Z_0 = 50 = \frac{V_o}{I_o} = \frac{5}{I_o}$

Summary

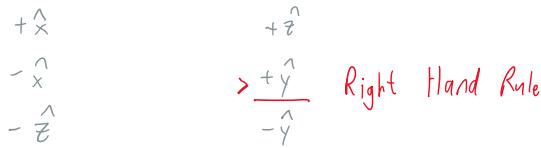Q1 Consider a TEM wave travelling down a transmission line in the $+z$ direction. If \vec{E} is in the $+x$ direction, what is the direction of \vec{H} ?



Q2 In a lossless transmission line, the characteristic impedance (Z_0) must be 0

True

> False

1.5 Power Loss in Transmission Lines

Low Loss Propagation

$R \ll \omega L$ and $G \ll \omega C$. Low Loss Model where G and R control Damping (Friction in Mechanics)

BASIC BEHAVIOUR:

- Substituting $\gamma = \alpha + j\beta$, our solution for the voltage, assuming real amplitudes V_o^+ , becomes

$$V_s = V_o^+ e^{-\gamma z} + V_o^- e^{\gamma z} \\ = V_o^+ e^{-\alpha z} e^{-j\beta z} + V_o^- e^{\alpha z} e^{j\beta z} \quad (\text{HB8, (48)})$$

- We multiply the phasor solution of (HB8, (48)) by $e^{j\omega t}$ and take the real part to get the real instantaneous voltage (assuming that the amplitudes, V_o^+ and V_o^- are real) as

$$V(z, t) = V_o^+ e^{-\alpha z} \cos(\omega t - \beta z) + V_o^- e^{\alpha z} \cos(\omega t + \beta z) \quad (\text{HB8, (49)})$$

damping forward wave
travelling reflected wave

$\gamma = \sqrt{R+j\omega L}(G+j\omega C)$
 (take the real part)

- Main idea: damped (attenuated) travelling wave in forward and backward directions. Simplifications $R \ll \omega L$ and $G \ll \omega C$ for α , β and Z_0 :

 - ① Use binomial expansion on γ to obtain simplified values for α and β
 - ② Use binomial expansion and the $\frac{1}{1+x}$ result for small x to get the final approximation for Z_0

- With our first Transmission Line model completed we move to power transmission!

Power Loss and dB

Wave: $V_s(z) = V_o e^{-\alpha z} e^{-j\beta z}$ HB8, G1
 $I_s(z) = I_o e^{-\alpha z} e^{-j\beta z} = \frac{V_o}{Z_0} e^{-\alpha z} e^{-j\beta z}$ HB8, G2

$$\langle P \rangle = \frac{1}{2} \operatorname{Re} (V_s(z) I_s^*(z)) \quad \text{HB8, G3}$$

$$\langle \rho \rangle = \frac{1}{2} \operatorname{Re} (V_s(z) I_s^*(z)) \quad \text{HB8, 63}$$

$$\begin{aligned} \langle \rho(z) \rangle &= \frac{1}{2} \operatorname{Re} \left[\frac{V_o V_o^*}{|z_0|} e^{-2az} e^{j\theta} \right] \\ &= \frac{1}{2} \frac{|V_o|^2}{|z_0|} e^{-2az} \cos \theta \end{aligned} \quad \text{HB8, 64}$$

$$\langle \rho(z) \rangle = \langle \rho(0) \rangle e^{-2az} \quad \text{HB8, 65} \quad \langle \rho(0) \rangle = \frac{1}{2} \frac{|V_o|^2}{|z_0|} \cos \theta$$

$$\frac{\langle \rho(z) \rangle}{\langle \rho(0) \rangle} = e^{-2az} = 10^{-Kaz} \quad \text{HB8, 66}$$

$$\text{set } az = 1 \rightarrow e^{-2} = 10^{-K} = K = \log_{10}(e^2) = 0.869 \quad \text{HB8, 67}$$

$$\text{Power Loss (dB)} = 10 \log_{10} \left[\frac{\langle \rho(0) \rangle}{\langle \rho(z) \rangle} \right] = 8.69 \propto z \quad \text{HB8, 68}$$

$$8.69 \frac{dB}{N_p} \cdot \frac{1}{m} \cdot m$$

Q1 Given a voltage wave travelling down a transmission line: $V_s = V_o e^{-az} e^{-j\beta z}$.

If $V_o = 5V$, $a = 0.1/m$, what is the voltage amplitude at the location $5m$?

$$V_s = (5V) e^{-(0.1)(5)} = 3.03V$$

Q2 Consider the following voltage wave on a transmission line: $V_s = (5V) e^{-az} e^{-j\beta z}$ with $a = 0.001/m$ and $\beta = 50\pi$

After the wave travels for $100m$, what is the time averaged power dissipated?

$$\langle P_{100} \rangle = 0.0453 \text{ W} \quad \langle P_i \rangle = \frac{1}{2} \frac{V_i^2}{Z_0} = \frac{1}{2} (5) e^{-0.1(100)} / (50) = 0.2047 \quad \langle P(0) \rangle = \frac{V_0^2}{Z_0} = \frac{5^2}{50} = 0.5$$

$$\langle P_i \rangle = \langle P(0) \rangle - \langle P \rangle_{100}$$

$$> 0.5 -$$

Nepers vs dB

$$\text{Amplitude ratios: } 20 \log_{10} \left(\frac{A_2}{A_1} \right) \text{ dB}$$

$$u = \log_{10} \left(\frac{A_2}{A_1} \right), 10^u = \left(\frac{A_2}{A_1} \right), \ln 10^u = u \ln 10 = \ln \left(\frac{A_2}{A_1} \right)$$

$$\text{New ratios: } N_p \rightarrow \ln \left(\frac{A_2}{A_1} \right) N_p \quad (\text{waves } \propto e^{-az})$$

$$\ln \left(\frac{A_2}{A_1} \right) N_p = 20 \log_{10} \left(\frac{A_2}{A_1} \right) \text{ dB}$$

$$N_p = \frac{20 \log_{10} \left(\frac{A_2}{A_1} \right) \text{ dB}}{\ln \left(\frac{A_2}{A_1} \right)} = \frac{20u}{u \ln 10} \text{ dB} \approx 8.69 \text{ dB}$$

$$\# dB = 20 \log_{10} \left(\frac{A_{\text{source}}}{A_{\text{receiver}}} \right)$$

$$e^{\# \text{ Nepers}} = \frac{A_{\text{source}}}{A_{\text{receiver}}}$$

$$\text{Nepers} = \ln \left(\frac{A_{\text{source}}}{A_{\text{receiver}}} \right)$$

$$20 \log_{10} e^{\# \text{ Nepers}} = 20 \log_{10} \left(\frac{A_{\text{source}}}{A_{\text{receiver}}} \right)$$

$$\# dB = 20 \log_{10} e^{\# \text{ Nepers}}$$

SS

$$\# dB = 20 \log_{10} (3) \approx 10$$

1G Reflection and Standing Waves

Reflection Generation

> Basic equations for an incident wave and reflected wave given by

> Basic equations for an incident wave and reflected wave given by


$$V_s = V_i(z) + V_r(z)$$

$$= V_{oi} e^{-\alpha z} e^{-j\beta z} + V_{or} e^{\alpha z} e^{j\beta z}$$

HB 8, 70a, 70b

> The reflection will be caused by a load, Z_L , located at $z=0$ at the end of the line

* Consider the figure below

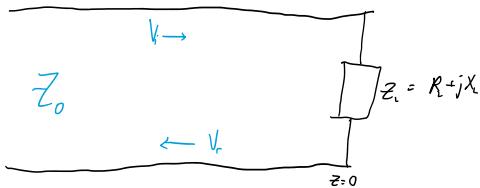

* At $z=0$, at the load, Z_L , the voltage and current are respectively:

$$V_L = V_{oi} + V_{or}$$

$$I_L = I_{oi} + I_{or}$$

$$\frac{V_L}{Z_L} = \frac{V_{oi}}{Z_L} = \frac{[V_{oi} + V_{or}]}{Z_L}$$

HB 8, 71, 72

* Now solve for the ratio $\frac{V_{or}}{V_{oi}}$

$$I_L = \frac{V_L}{Z_L} = \frac{[V_{oi} + V_{or}]}{Z_L} = \frac{1}{Z_L} [V_{oi} - V_{or}]$$

$$Z_L (V_{oi} + V_{or}) = Z_L (V_{oi} - V_{or})$$

$$Z_L \left(\frac{V_{or}}{V_{oi}} \right) = Z_L \left(\frac{V_{or}}{V_{oi}} \right)$$

$$Z_L (1 + \Gamma) = Z_L / (1 - \Gamma)$$

$$Z_L - Z_L = -Z_L \Gamma - Z_L \Gamma = (Z_L + Z_L) \Gamma$$

$$\Gamma = (Z_L - Z_0) / (Z_L + Z_0)$$

* Continuing,

$$\Gamma = \frac{V_{or}}{V_{oi}} = \frac{Z_L - Z_0}{Z_L + Z_0} = |\Gamma| e^{j\theta}$$

* The voltage at the load is the sum of the incident and reflected voltages at $z=0$. That ratio is the transmission coefficient:

$$\Gamma = \frac{V_L}{V_{oi}} = \frac{[V_{oi} + V_{or}]}{V_{oi}} = \frac{[V_{oi} + \Gamma V_{oi}]}{V_{oi}} = 1 + \Gamma$$

HB 8, (74, 75)

Q1 From this video, $\Gamma = |\Gamma| e^{j\theta}$.

When $|\Gamma| \neq 0$ and $\theta \neq m\pi$ where $m \in \mathbb{Z}$:

Γ has an imaginary component which indicates loss in the form of heat dissipation at the boundary

> Γ has an imaginary component which introduces a phase shift of the reflected wave

Video Recap: The reflection coefficient between a transmission line and the load, Γ , is defined as

$$\Gamma = \frac{V_{or}}{V_{oi}} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma = \frac{V_{or}}{V_{oi}} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

It is clear from the 1st part of the equation that Γ is a ratio between the amplitudes of the reflection and the incident voltage waves ($V_{or} = \Gamma V_{oi}$)

Q2 Given that $V_{oi} = 5V$ and $\Gamma = 0$, what is V_{or} ?

5V

> 0V

$$V_{or} = 0 \cdot 5$$

2.5V

$$= 0$$

Q3 What is the physical interpretation when $\Gamma = 0$?

> There is no reflection

The voltage wave is partially reflected

The voltage wave is fully reflected

Q4 Given that $V_{oi} = 5V$ and $\Gamma = -0.5$, what is V_{or} ?

> -2.5V

2.5V

5V

Q5 What is the physical interpretation when $\Gamma = -0.5$?

The voltage wave is partially reflected with no polarity change at the boundary

> The voltage wave is partially reflected with reversed polarity at the boundary

The voltage wave is fully reflected

Power Reflection and Transmission

- Using the Reflection Coefficient to Find the Time-Averaged Power Transfer

$$\Gamma = \frac{V_{or}}{V_{oi}} = \frac{Z_L - Z_0}{Z_L + Z_0} = |\Gamma| e^{j\theta}$$

$$T = \frac{V_o}{V_{oi}} = \frac{[V_{oi} + V_{or}]}{V_{oi}} = \frac{[V_{oi} + \Gamma V_{oi}]}{V_{oi}} = [1 + \Gamma]$$

- The application of these coefficients should be straightforward with V and I waves (e.g. reflected Voltage V_{or} is simply ΓV_{oi}). But what about the reflection and transmission of power?
- Let's examine the incident and reflected power at the boundary between a lossless transmission line and a load (or between two lossless transmission lines with different characteristic impedances). The incident time-averaged power can be expressed by:

$$\langle P_i \rangle = \frac{1}{2} R \left\{ \frac{V_o V_{oi}^*}{|Z_0|} e^{j\theta} \right\} = \frac{1}{2} \frac{|V_o|^2}{|Z_0|} \cos \theta$$

and the reflected time-averaged power by (note the voltage amplitude is simply substituted with the reflected voltage amplitude):

and the reflected time-averaged power by (note the voltage amplitude is simply substituted with the reflected voltage amplitude):

$$\langle P_r \rangle = \frac{1}{2} R \left\{ \frac{(\Gamma V_0)(\Gamma^* V_0^*)}{|Z_0|} e^{j\theta} \right\} = \frac{1}{2} \frac{|\Gamma|^2 |V_0|^2}{|Z_0|} \cos \theta$$

- The ratio between reflected & incident power is

$$\frac{\langle P_r \rangle}{\langle P_i \rangle} = |\Gamma|^2 \quad \text{everything else cancels out!}$$

- Through similar procedures, one can conclude that the transmission coefficient can be expressed as

$$\frac{\langle P_t \rangle}{\langle P_i \rangle} = 1 - |\Gamma|^2$$

Transmission lines A and B with different characteristic impedances, Z_{A0} and Z_{B0} , are connected in series. The reflection coefficient at the connection is given by $\Gamma = 0.2$. For an incident time-averaged power of 10W, find:

Q1 $\langle P_r \rangle = 0.4 \text{ W}$ $P_i = 10 \text{ W}$, $\frac{P_r}{P_i} = 0.2^2 = 0.04$, $P_r = 0.4$


Q2 $\langle P_t \rangle = 9.6 \text{ W}$ $\frac{P_t}{P_i} = 0.96$, $P_t = 9.6$

Consider the same setup as above but this time $\Gamma = 0.1 + j0.1$. Incident power remains as 10W.

Q3 $\langle P_r \rangle = 0.2 \text{ W}$ $|\Gamma|^2 = 0.02$, $\frac{\langle P_r \rangle}{\langle P_i \rangle} = 0.02$, $\langle P_r \rangle = 0.2$

Q4 $\langle P_t \rangle = 9.8 \text{ W}$ $\frac{\langle P_t \rangle}{\langle P_i \rangle} = 0.98$, $\langle P_t \rangle = 9.8$

VSWR - Engineering Setting

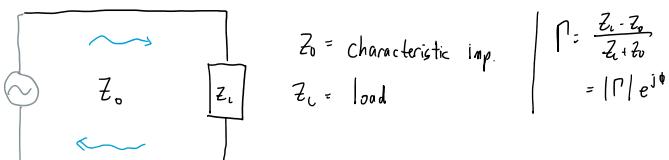


$$Z_0 = \text{characteristic imp.} \quad \left| \begin{array}{l} \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \\ = |\Gamma| e^{j\phi} \end{array} \right.$$

① $Z_L = Z_0$ $\Gamma = 0$ — no reflection

② $Z_L \neq Z_0$

VSWR - Physics Setting

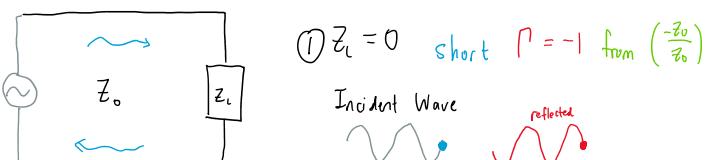

① $Z_L = 0$ short $\Gamma = -1$ from $(-\frac{Z_0}{Z_0})$



② $Z_L \neq 0$

???

VSWR - Math Intuition

$$\Gamma = r + jx = -i\beta z \quad \text{and} \quad -i\beta z \Gamma = 2i\beta z^2$$

VSWR - Math Intuition

$$V_{ST}(z) = V_o e^{-j\beta z} + |V_s| e^{j\beta z} = V_o e^{-j\beta z} [1 + |V_s| e^{2j\beta z}]$$

$$|V_s| = \frac{Z_L - Z_0}{Z_L + Z_0} = |V_s| e^{j\phi}$$

$$V_s(z) = V_o e^{-j\beta z} [1 + |V_s| e^{j(2\beta z + \phi)}]$$


Example: Open Circuit Load:

$$|V_s| = 1 \quad \text{and} \quad \phi = 0 \quad Z_L \rightarrow \infty$$

$$V_{ST} = V_o e^{-j\beta z} + |V_o| e^{j\beta z} = V_o \cdot 2 \cos(\beta z)$$

$$\text{Conclusion: } V(z,t) = R \{ V_{ST} e^{j\omega t} \} = 2 V_o \cos(\beta z) \cos(\omega t)$$

VSWR - Engineering Application
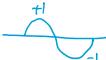
$$V_s(z) = V_o e^{-j\beta z} [1 + |V_s| e^{j(2\beta z + \phi)}]$$


When is the amplitude of V_{ST} max?

$$V_o (1 + |V_s|)$$

$$V_o (1 - |V_s|)$$

Implication: Gives us access to the phase of $|V_s| \rightarrow \phi$

VSWR: Voltage Standing Wave Ratio

We can find our load impedance by measuring the VSWR and the phase of the reflection coefficient

$$\text{VSWR} = \frac{1 + |V_s|}{1 - |V_s|}$$

Q1 VSWR is

> Infinite if all incident waves are reflected

> 1 if there is no reflected wave

Q2 Assuming that you can measure the voltage at any point of a transmission line, how can the amplitude of the reflection coefficient, $|V_s|$, be acquired if Z_0 and Z_L are both unknown?

Noticing that VSWR is the ratio between max and min voltage amplitudes, you measure the voltages at multiple points and find the maximum & minimum oscillation amplitudes. You think $|V_s| = \frac{S+1}{S-1}$ where S is the VSWR and you successfully calculate $|V_s|$ and live happily ever after.

> Noticing that VSWR is the ratio between max and min voltage amplitudes, you measure the voltages at multiple points and find the maximum & minimum oscillation amplitudes. You think $|V_s| = \frac{S+1}{S-1}$ where S is the VSWR and you successfully calculate $|V_s|$ and live happily ever after.

until you successfully calculate it and live happily ever after.

> Noticing that VSWR is the ratio between max and min voltage amplitudes, you measure the voltages at multiple points and find the maximum & minimum oscillation amplitudes. You think $|P| = \frac{s-1}{s+1}$ where s is the VSWR and you successfully calculate $|P|$ and live happily ever after.

Don't know

$$s = \frac{1+|P|}{1-|P|}$$

42

Q3 Consider a transmission line that is terminated by a mismatched load such that reflection exists within the line ($Z_L \neq Z_0$).

The maximum voltage amplitude has been measured to be 85V, and the minimum voltage amplitude has been measured to be 17V. What is the VSWR?

$$\frac{85V}{17V} = 5$$


Q4 For a system where VSWR is known to be 7.1, what is the magnitude of the reflection current $|P|$?

$$|P| = \frac{7.1-1}{7.1+1} = \frac{6.1}{8.1} = 0.753$$

1.7 Black Magic Design : the Smith Chart

Input Impedance

Normal Circuits:

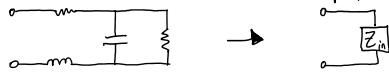


T-Lines:



$$Z_{in} = \frac{V}{I} = \frac{V_o^+ e^{-\gamma z} + V_o^- e^{\gamma z}}{\frac{V_o^+}{Z_0} e^{-\gamma z} - \frac{V_o^-}{Z_0} e^{\gamma z}}$$

$$\gamma = j\beta$$

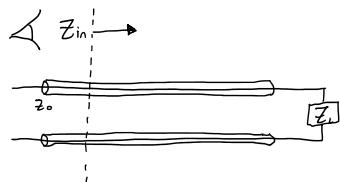Input impedance looking into an arbitrary point of a transmission line system looking towards the load



Q1 In the video, we've ended with the input impedance expression

$$Z_{in} = \frac{V}{I} = \frac{V_o^+ e^{-\gamma z} + V_o^- e^{\gamma z}}{\frac{V_o^+}{Z_0} e^{-\gamma z} - \frac{V_o^-}{Z_0} e^{\gamma z}}$$

where in this case $\gamma = j\beta$ as we're considering a lossless line, and $\beta = \frac{2\pi}{\lambda}$. Substituting $\beta = \frac{2\pi}{\lambda}$ and $V_o^- = |P| V_o^+$ into the expression, which of the following expressions do we acquire?

$$Z_{in} = \frac{1}{Z_0} \frac{e^{-j\frac{2\pi}{\lambda} z} + P e^{j\frac{2\pi}{\lambda} z}}{e^{j\frac{2\pi}{\lambda} z} - P e^{j\frac{2\pi}{\lambda} z}}$$

$$Z_{in} = Z_0 \frac{1+P}{1-P}$$

$$Z_{in} = Z_0 \frac{e^{-j\frac{2\pi}{\lambda} z} + P e^{j\frac{2\pi}{\lambda} z}}{e^{-j\frac{2\pi}{\lambda} z} - P e^{-j\frac{2\pi}{\lambda} z}}$$

$$Z_{in} = Z_0 \frac{(1+P)e^{j\frac{2\pi}{\lambda} z}}{(1-P)e^{-j\frac{2\pi}{\lambda} z}}$$

$$t_n = t_0 \frac{e^{-j\frac{2\pi}{\lambda} z}}{(1-\Gamma)e^{j\frac{2\pi}{\lambda} z}}$$

Q2 Consider the Z_{in} expression from the previous answer. When substituting z by $z + \frac{\lambda}{2}$, how does input impedance change?
Hint: What can $e^{j\pi}$ and $e^{-j\pi}$ be simplified to?

> Not at all

The magnitude of the input impedance increases

AC transmission becomes DC

loss (α) gets introduced

Q3 Assume that the Z_{in} is known at $z = \frac{\lambda}{8}$ for a line that is 1λ long. What is the next location where the input impedance is the same?


$$z = \frac{6}{8}\lambda$$

$$z = \frac{4}{8}\lambda$$

> $z = \frac{5}{8}\lambda$

$$z = \frac{7}{8}\lambda$$

Constructing the Smith Chart

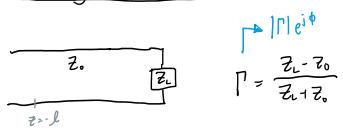

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

normalize

$$\textcircled{1} \quad z_i = \frac{Z_L}{Z_0}$$

$$\textcircled{2} \quad \Gamma = \frac{Z_L - 1}{Z_L + 1}$$

$$z_i = \frac{1+\Gamma}{1-\Gamma}$$

$$V_s(z) = V_0 e^{-j\beta z} + \Gamma V_0 e^{j\beta z}$$

$$= V_0 e^{-j\beta z} (1 + \Gamma e^{2j\beta z})$$

$$V_s(z = -l) = V_0 e^{j\beta l} (1 + \Gamma e^{-2j\beta l})$$


$$I_s(z = -l) = \frac{V_0 e^{j\beta l}}{Z_0} (1 - \Gamma e^{-2j\beta l})$$

wave impedance

$$Z_w \text{ (at } z=0) = Z_0 \cdot \frac{1+\Gamma}{1-\Gamma}$$

$$Z_{in} \text{ (at } z=0) = \frac{1+\Gamma}{1-\Gamma}$$

normalized wave impedance

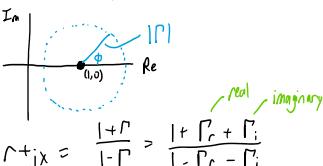


When $l = 0 \rightarrow$ starting point

at Load: $Z_{in} = \frac{1+\Gamma}{1-\Gamma}$

$$\Gamma = |\Gamma| e^{j\phi}$$

at any z : $Z_{in} = \frac{1+|\Gamma| e^{j(\phi-2\beta z)}}{1-|\Gamma| e^{j(\phi-2\beta z)}}$

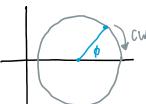

$$r + jx = \frac{1 + \Gamma_r + j\Gamma_i}{1 - \Gamma_r + j\Gamma_i} \times \frac{1 - \Gamma_r + j\Gamma_i}{1 + \Gamma_r + j\Gamma_i} = \frac{1 - \Gamma_r + j\Gamma_r + \Gamma_r - \Gamma_r^2 + \Gamma_r \times j\Gamma_i + j\Gamma_r - j\Gamma_r \Gamma_i - \Gamma_i^2}{(1 + \Gamma_r)^2 + \Gamma_i^2}$$

$$r = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{1 - 2\Gamma_r + \Gamma_r^2 + \Gamma_i^2}, \quad x = \frac{2\Gamma_i}{1 - 2\Gamma_r + \Gamma_r^2 + \Gamma_i^2}$$

$$r\Gamma_r^2 + \Gamma_r^2 - 2r\Gamma_r + r\Gamma_i^2 = 1$$

$$\Gamma_r^2(r+1) - 2r\Gamma_r + \Gamma_i^2(r+1) = 1 - r$$

$$\Gamma_r^2 - \frac{2r\Gamma_r}{r+1} + \Gamma_i^2 = \frac{1-r}{r+1}$$

$$\Gamma_r^2 - \frac{2r}{r+1} \Gamma_r + \left(\frac{r}{r+1}\right)^2 + \Gamma_i^2 = \frac{(1-r)}{(1+r)} + \frac{r^2}{(1+r)^2} = \frac{\frac{1-r}{r+1}(1+r) + r^2}{(1+r)^2} = \frac{1}{(1+r)^2}$$

$$\Gamma_r^2 = \frac{2r|t|}{r+1} + |t|^2 = \frac{1-r}{r+1}$$

$$\Gamma_r^2 - \frac{2r}{r+1} \Gamma_r + \left(\frac{r}{r+1}\right)^2 + |t|^2 = \frac{(1-r)}{(1+r)} + \frac{r^2}{(r+1)^2} = \frac{(1-r)(1+r) + r^2}{(1+r)^2} = \frac{1}{(r+1)^2}$$

$$\left(\frac{\Gamma_r}{r+1}\right)^2 + |t|^2 = \frac{1}{(r+1)^2}$$

two families of Circles!


Using the Smith Chart

$$Z_i = 50 + j100 \Omega, Z_0 = 50 \Omega$$

$$Z_o = 25 - j50 \Omega, Z_0 = 50 \Omega$$

$$z_c = 1.0 + j2.0$$

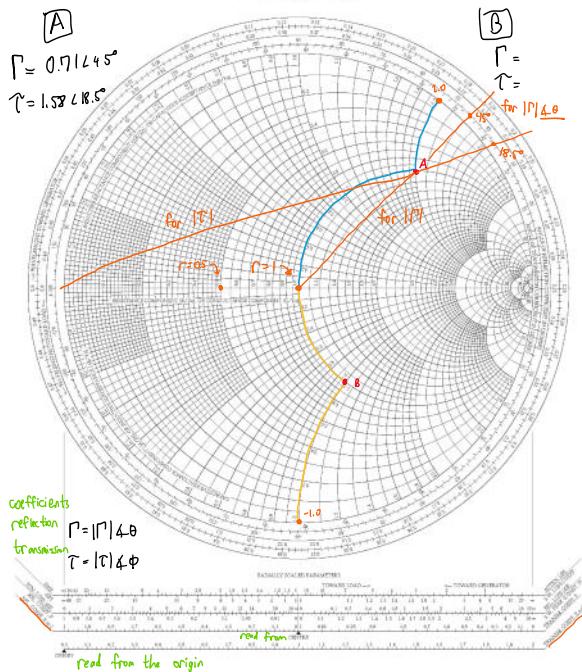The Complete Smith Chart
Black Magic Design




Admittances on the Smith Chart, Necessary for Analysis

$$\text{Admittance } Y = \frac{1}{Z}$$

$$Y = G + j\beta$$

$$Z = R + jX$$

Short Circuit Load on T-Line - Analysis

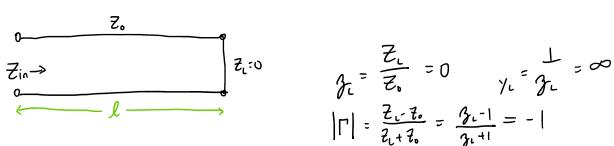

$$\gamma_L = \frac{Z_L}{Z_0} = 0 \quad y_L = \frac{1}{Z_L} = \infty$$

$$|\Gamma| = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Z_0 - 1}{Z_0 + 1} = -1$$

$$\gamma_{in} = \frac{1 + \Gamma e^{-2j\beta l}}{1 - \Gamma e^{-2j\beta l}} = \frac{e^{j\beta l} - e^{-j\beta l}}{e^{j\beta l} + e^{-j\beta l}} = \frac{2j \sin \beta l}{2 \cos \beta l} = j \tan \beta l$$

$$y_{in} = \frac{1}{\gamma_{in}} = \frac{1}{j \tan \beta l} = -j \cot \beta l \quad 0 < l < \frac{\lambda}{4} \quad \beta l = 0, \gamma_{in} = \infty$$

keep cot in "same quadrant"

Stub Matching

$$\begin{aligned} \text{Max } V &= V_o^+ e^{-j\beta z} + \Gamma V_o^+ e^{j\beta z} \\ \text{Min } I &= \frac{V_o^+ e^{-j\beta z} - \Gamma V_o^+ e^{j\beta z}}{Z_0} \end{aligned}$$

Get ratio

$$\begin{aligned} \frac{V_{max}}{V_{min}} &= \frac{V_o^+ e^{-j\beta z} (1 + \Gamma e^{j\beta z})}{V_o^+ e^{-j\beta z} (1 - \Gamma e^{j\beta z})} \rightarrow \frac{V_o^+ (1 + |\Gamma|)}{V_o^+ (1 - |\Gamma|)} \\ \frac{I_{max}}{I_{min}} &= \frac{V_o^+ e^{-j\beta z} (1 - \Gamma e^{j\beta z})}{Z_0} \rightarrow \frac{V_o^+ (1 - |\Gamma|)}{Z_0} \end{aligned}$$

$$\begin{aligned} Z_{max} &= \frac{V_{max}}{I_{max}} = \frac{1 + |\Gamma|}{1 - |\Gamma|} (Z_0) \\ Z_{max} &= \frac{Z_{max}}{Z_0} = \frac{1 + |\Gamma|}{1 - |\Gamma|} \text{ normalized} \end{aligned}$$